

FY_EEEE_Theory_IA2_Quiz

Total points **13/20** ?

FY BTech_EEEE_Theory_IA2_Quiz

The respondent's email (**rajat.kumar@somaiya.edu**) was recorded on submission of this form.

Enter your Name *

Rajat Kumar

Enter Your Roll Number *

16014224054

Enter your Division *

☐ C1

☐ C2

☐ C3


☐ C4

☒ C5

☐ C6

- ✓ 1) In the following circuit, what should be the value of R to absorb the maximum power from the source? *

1/1

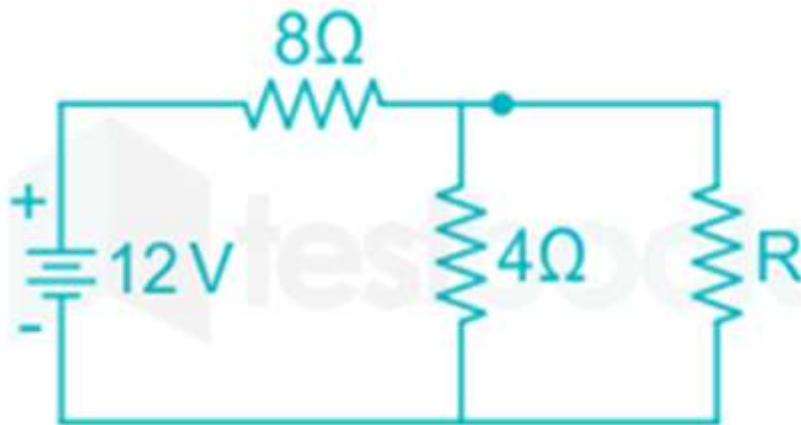

☐ $3/8\ \Omega$

☒ $8/3\ \Omega$



☐ $4\ \Omega$

☐ $8\ \Omega$

- ✓ 2) In a Full wave rectifier what is the average value of the voltage at the output of the rectifier? *

1/1

☐ $V_m/2$

☒ $2V_m/\pi$



☐ V_m/π


☐ $V_m/2\pi$

✗ 3) Refer the following circuit diagram:

*

0/1

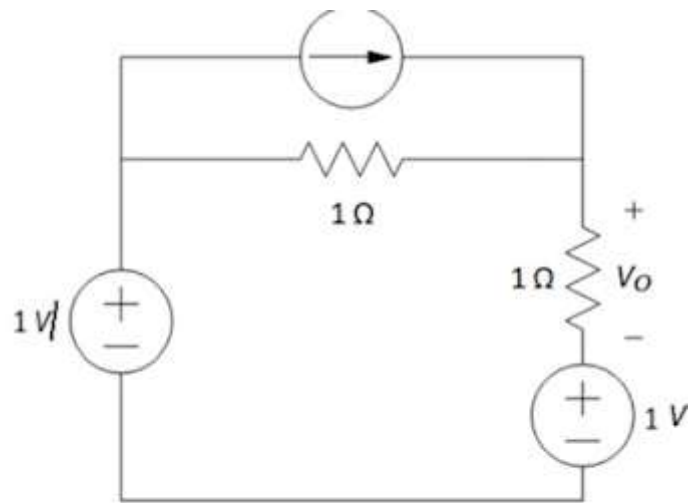Calculate value of voltage V_o across $1\ \Omega$ resistor



☐ -1.5 V

☐ -0.5 V

☒ 0 V

✗

☐ 0.5 V

Correct answer

☒ 0.5 V

✓ 4) The Thevenin voltage is the_____ *

1/1

☐ Short circuit voltage

☒ Open circuit voltage

✓

☐ Neither open circuit nor short circuit voltage

☐ Both Open circuit and short circuit voltage

✓ 5) If Current and Voltage are 90 Degree Out of Phase, Then The Power (P) *1/1 will be_____.

☒ Zero ✓

☐ Maximum

☐ Minimum

☐ Normal

✗ 6) In a half wave rectifier, the diode conducts for *

0/1

☒ Half cycle ✗

☐ None of these

☐ Full cycle

☐ Alternate Half cycle

Correct answer

☒ Alternate Half cycle

✗ 7) The reverse current effect damages the junction in _____ *0/1
diode

☒ Zener diode ✗

☐ None of these

☐ LED

☐ PN Junction diode

Correct answer

☒ PN Junction diode

✗ 8) ----- breakdown voltage is directly proportional to the temperature * 0/1

☐ None of the above

☒ Zener ✗

☐ Both above

☐ Avalanche

Correct answer

☒ Avalanche

✓ 9) An ideal diode in forward bias have _____ resistance * 1/1

☐ None of the above

☐ Finite

☐ Infinite

☒ Zero ✓

✓ 10) The half-wave rectifier output DC voltage calculated by _____ * 1/1

☐ $V_{\text{peak}}/2\pi$

☐ $2V_{\text{peak}}/\pi$

☐ $V_{\text{peak}}/4\pi$

☒ V_{peak}/π



✓ 11) Three similar coils each of resistance $20\ \Omega$ and inductance of $0.5\ \text{H}$, *1/1
are connected in star to a three phase $50\ \text{Hz}$, $400\ \text{V}$ supply then what is
the value of phase voltage

☐ $400\ \text{V}$

☒ $230.94\ \text{V}$



☐ $692\ \text{V}$

☐ $440\ \text{V}$

✗ 12) In the measurement of 3-phase power using two wattmeter method, *0/1
the value of phase angle when the two wattmeter reads equal reading is

☒ 90

✗

☐ 60

☐ 45

☐ 0

Correct answer

☒ 0

✓ 13) In NPN BJT transistor which of the following terminal defines P-type *1/1

☐ Collector


☒ Base

✓

☐ Gate

☐ Emitter

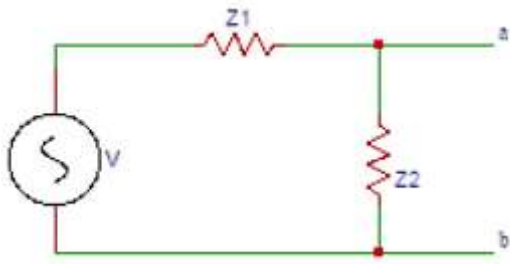✓ 14) The Norton's equivalent impedance (Z_N) in the circuit shown below is: *1/1



☐ $(Z_1 + Z_2)/Z_1$

☒ $Z_1 Z_2 / (Z_1 + Z_2)$ ✓

☐ $Z_1 + Z_2$

☐ $(Z_1 + Z_2)/Z_2$

☐ Other: _____

✗ 15) If the resistance of the load is double the resistance of the source in a circuit, the power transferred to the load is _____ *0/1

☐ Double the maximum power

☐ One fourth of the maximum power

☐ Equal to the maximum power

☒ Half of the maximum power ✗

Correct answer

☒ Double the maximum power

✓ 16) The Maximum Power Transfer Theorem is based on the concept of *1/1

☒ Thevenin's Theorem ✓

☐ Kirchoff's Law

☐ Ohm's Law

☐ Superposition Theorem

✓ 17) The efficiency and ripple factor of center tap full wave rectifier is *1/1

☐ 28.7% and 1.21

☐ 69.3% and 0.48

☒ 81.2% and 0.48 ✓

☐ 40.6% and 1.21

✓ 18) In the P-N junction at thermal equilibrium, the space charge region is a zone with a net charge provided by *1/1

☐ Minority charge carriers

☐ both majority and minority charge carriers

☐ Majority charge carriers

☒ Immobile ions ✓

✓ 19) Which of the following BJT terminal controls the current flow *

1/1

☒ Base



☐ Drain

☐ Collector

☐ Emitter

✗ 20) In which of the following region do BJT operates in forward bias? *

0/1

☒ Active



☐ Cut-off

☐ Both a and c

☐ Saturation

Correct answer

☒ Both a and c

This form was created inside of Somaiya Vidyavihar.
Does this form look suspicious? [Report](#)

Google Forms