

Course Name:	Elements of Electrical and Electronics Engineering Laboratory	Semester:	I/II
Date of Performance:	13/09/2024	Batch No:	C5-3
Student Name:	Rajat Kumar	Roll No:	54
Faculty Sign & Date:		Grade/Marks:	/ 20

Experiment No: 3

Title: Thevenin's Theorem & Norton's Theorem


Aim and Objective of the Experiment:

- To Verify for Thevenin's Theorem for the circuit
- To Verify Norton Theorem for the Circuit.


COs to be achieved:

CO1: Analyze resistive networks excited by DC sources using various network theorems.


Circuit Diagram:

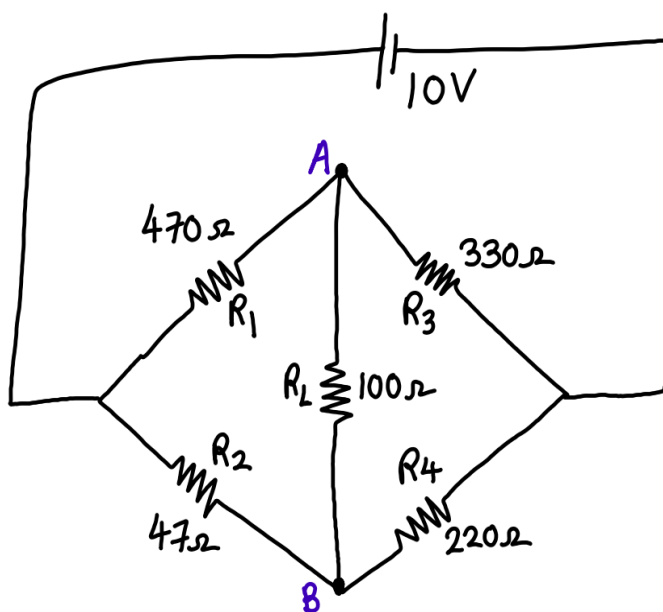


Task 1: Circuit Diagram to measure R_{TH}/R_N :

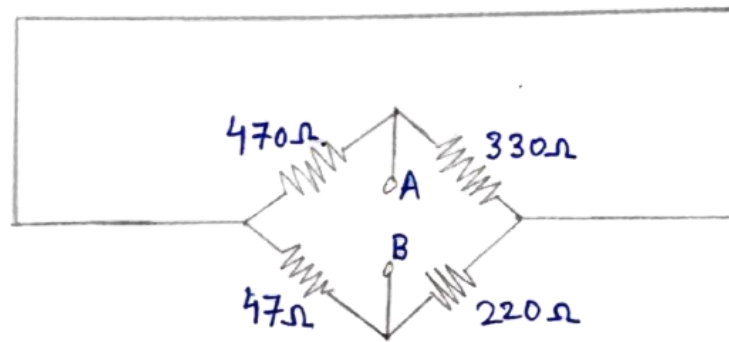

Task 2: Circuit Diagram to measure V_{TH} :

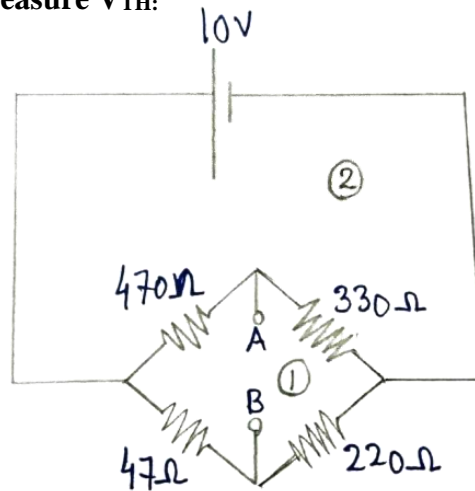

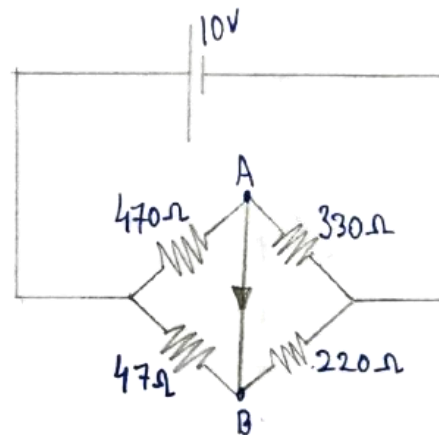Task 3: Circuit Diagram to measure I_{SC} :



Stepwise-Procedure:

Thevenin's Theorem:

1. Connect the circuit as shown in the circuit diagram.
2. Set 10V and measure open circuit voltage V_{Th} across load terminals A and B.
3. Replace all voltage sources by Short circuit and measure R_{Th} across terminals A and B as per the circuit diagram shown in the figure.
4. Draw Thevenin's equivalent circuit and determine the value of load current from it.
5. Verify the results theoretically.

Norton's Theorem:

1. Connect the circuit as shown in the circuit diagram.
2. Set the voltages 10V
3. Remove the load resistance and measure the short circuit current I_{SC} through A and B terminals.
4. Replace all the voltage sources by Short circuit and measure R_{Th} across terminals A and B as per the circuit diagram shown in the figure.
5. Draw Norton's equivalent circuit and determine the value of load current.
6. Verify the results theoretically

Calculations:

1. To Calculate R_{Th}/R_N :

$$\begin{aligned}
 &\rightarrow R_1 \parallel R_3 \\
 &\therefore 470 \parallel 330 = \frac{470 \times 330}{800} \\
 &= 193.87 \Omega \dots (1) \\
 &\rightarrow R_2 \parallel R_4 \\
 &\therefore 47 \parallel 220 = \frac{47 \times 220}{267} \\
 &= 38.72 \Omega \dots (2) \\
 &\rightarrow \text{Since, (1) \& (2) ; both are in series -} \\
 &\therefore (1) + (2) \Rightarrow R_{th} = 232.6 \Omega
 \end{aligned}$$

2. To Calculate V_{Th} :

$$\begin{aligned}
 V_{AB} &= 470(I_1 - I_2) + 47I_1 = 517I_1 - 470I_2 \dots (3) \\
 \text{Loop across mesh - (1)} \\
 \Rightarrow -470(I_1 - I_2) - 330(I_1 - I_2) - 220I_1 - 47I_1 &= 0 \\
 \therefore -1067I_1 + 800I_2 &= 0 \dots (4) \\
 \text{Now, Loop across mesh - (2)} \\
 \Rightarrow -330(I_2 - I_1) - 470(I_2 - I_1) &= 10 \\
 \therefore 800I_1 - 800I_2 &= 10 \dots (5) \\
 \text{From (4) \& (5)} &\therefore V_{AB} = 517(-0.0375) - 470(-0.05) \\
 I_1 = -0.0375 &= -19.39 + 23.5 \\
 I_2 = -0.05 &= 4.11V \\
 \therefore V_{AB} = V_{th} &\therefore V_{th} = 4.11V
 \end{aligned}$$

3. To Calculate I_N/I_{sc} :

$$I_{sc} = I_N = \frac{V_{th}}{R_{th}}$$

$$\because R_{th} = R_N \Rightarrow \therefore I_{sc} = \frac{V_{th}}{R_N} = \frac{4.11}{232.6} = 17.66 \text{ mA}$$

$$\therefore I_{sc} = 17.66 \text{ mA}$$


4. To Calculate I_L :

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{R_N \times I_{sc}}{R_{th} + R_L} = \frac{4.11}{332.6}$$


$$\therefore I_L = 12.35 \text{ mA}$$

Observation Table:

	V_{TH} (V)	R_{TH} / R_N (Ω)	I_N (mA)	I_L (mA)
Theoretical value	4.11V	232.6 Ω	17.66 mA	12.35 mA
Practical value	4.12V	231.8 Ω	17.54 mA	12.41 mA

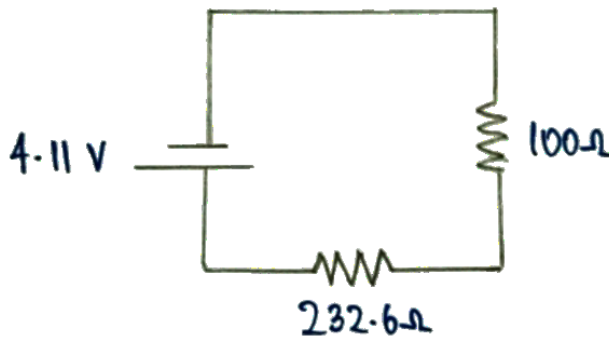Draw Thevenin's Equivalent circuit


Draw Norton's Equivalent circuit

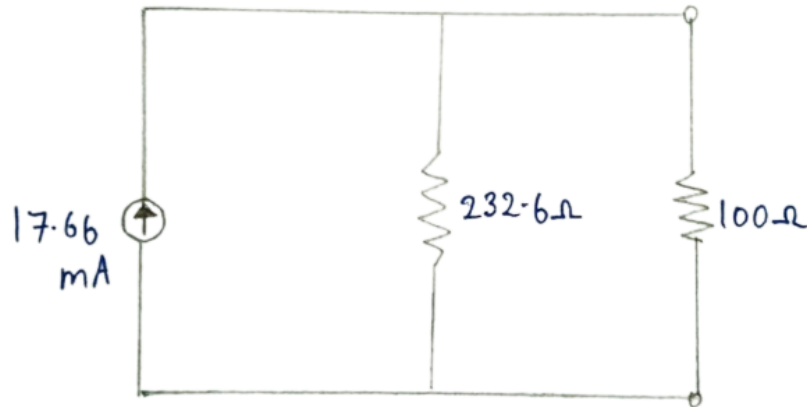

Conclusion:

By performing the experiment, we can verify that Thevenin's and Norton's theorems provide methods for simplifying complex circuits and reducing them to their equivalent forms, facilitating easier analysis and confirming the theorems' accuracy in practical applications.

Signature of faculty in-charge with Date: