

Course Name:	Elements of Electrical and Electronics Engineering	Semester:	I
Exam:	EEEE IA1	Division:	C5
Name:	Rajat Kumar	Branch:	AI & DS
Roll No:	16014224054	Roll No:	54

Q2. Calculate the current through $4\ \Omega$ resistor using Norton's theorem. In the circuit shown in figure 2, the value of R_1 will be the **last two digits of roll no. time's Ω**

For eg: For Roll no: 1000020, then $R_1 = 20\ \Omega$. If your last digits are from 01 to 10, kindly add 10 to your last two digits, so roll no with last two digits with 01 will become 11, then $R_1 = 11\ \Omega$

(EVEN ROLL NO ATTEMPT Q2)

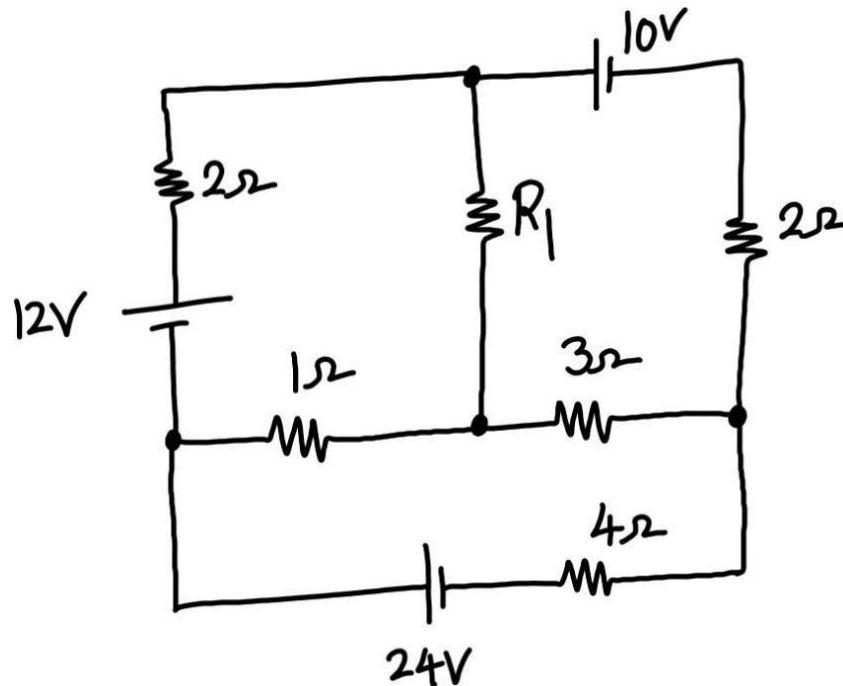



Figure 2

- a) Simulate the circuit show in figure 2, using *LTSpice* software and measure I_N , R_N and I_L .


Circuit Diagram:

Rajat Kumar
 C5-3-54 (AI&DS)
 16014224054

Given Circuit Diagram

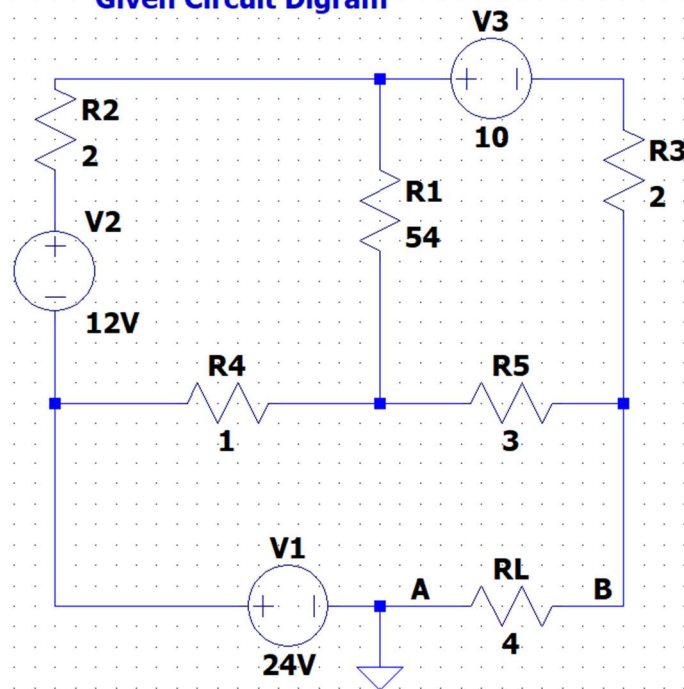


To find Norton's Current (I_N):

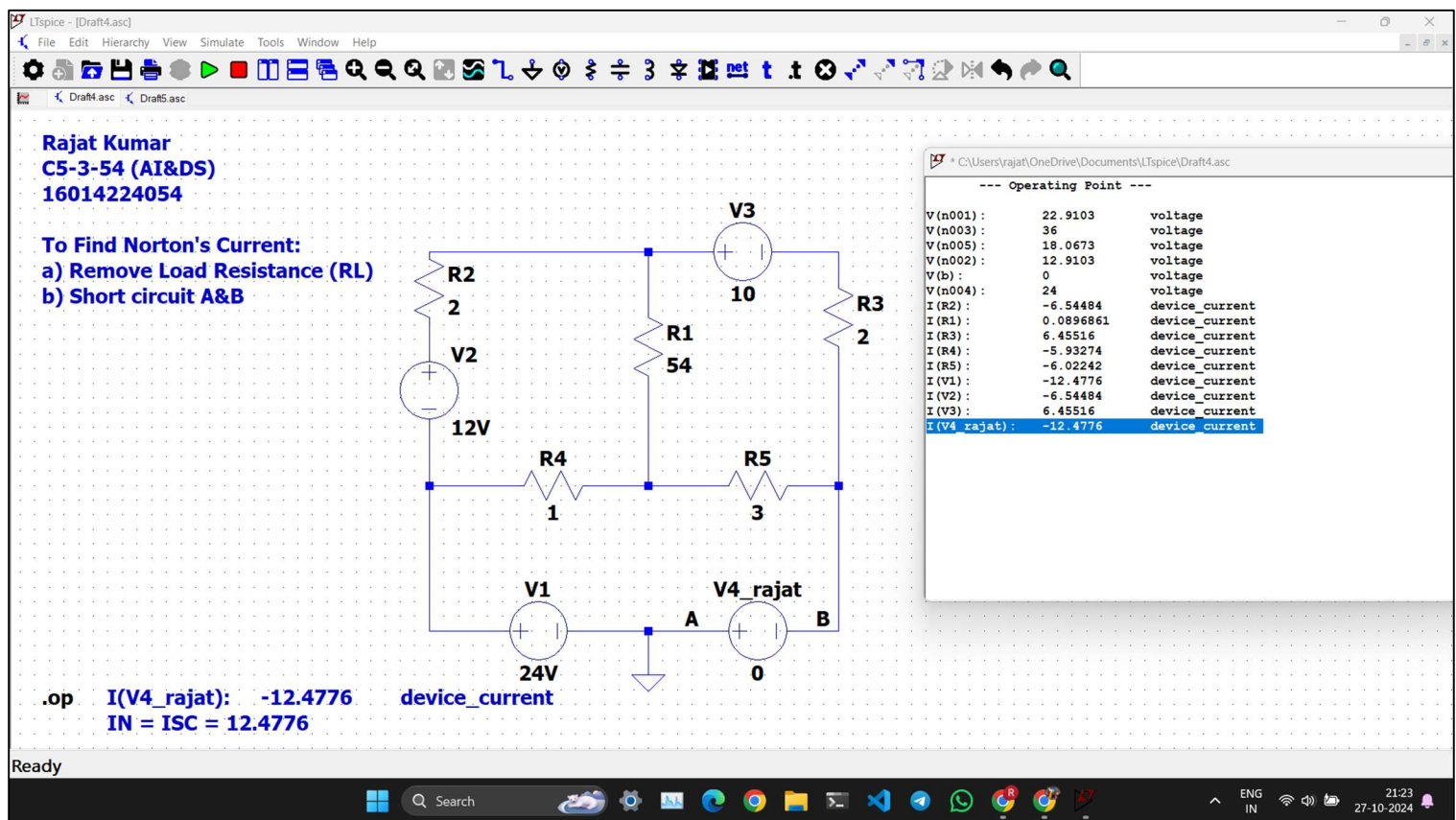

To find Norton's Resistance (R_N):

Rajat Kumar
C5-3-54 (AI&DS)
16014224054

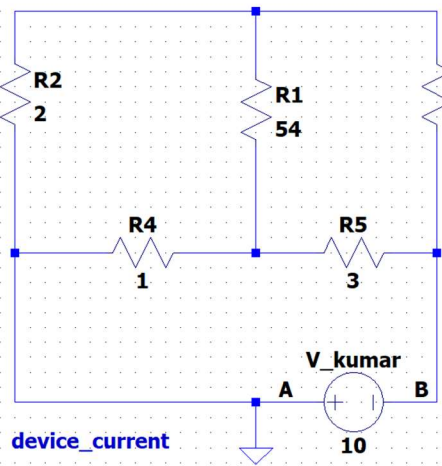To find Norton's Resistance
a) Remove RL
b) Short Circuit Voltage Sources




$I(V_kumar): -5.01121$ device_current
 $V = 10V$
 $R_N = 10 / 5.01121 \Rightarrow R_N = 1.9955$

--- Operating Point ---

Variable	Value	Unit
V(m001)	-4.95516	voltage
V(m002)	-2.53363	voltage
V(b)	-10	voltage
I(R2)	-2.47758	device_current
I(R1)	-0.044843	device_current
I(R3)	2.52242	device_current
I(R4)	-2.53363	device_current
I(R5)	-2.48879	device_current
I(V_kumar)	-5.01121	device_current

Ready

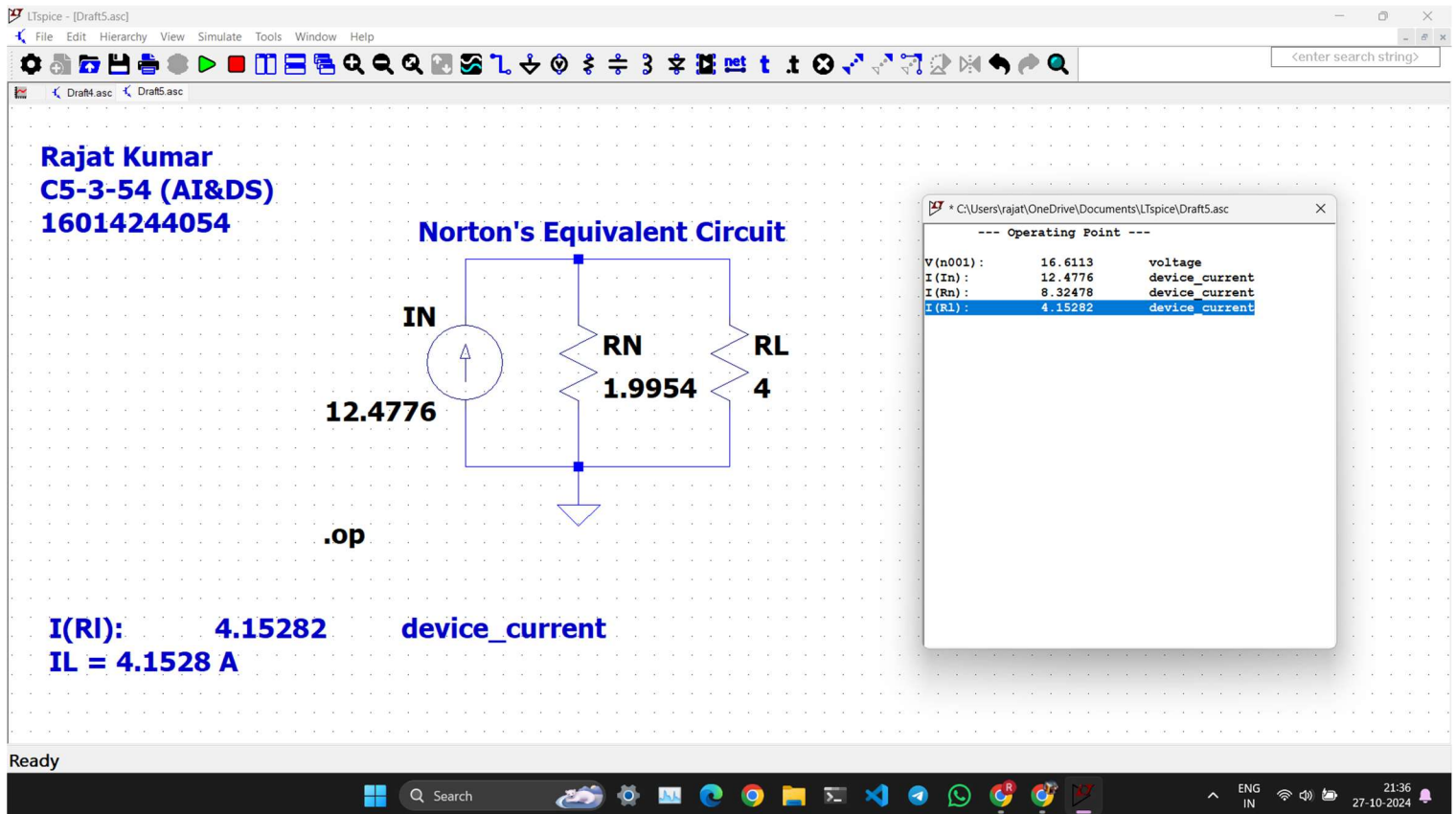To Find Required Load Current (I_L) across Load Resistance ($4\ \Omega$):



b) Also Solve the numerical theoretical and measure I_N , R_N and current through $4\ \Omega$ load resistor (I_L)

16014224054

Batch: C5-3 Roll No.: 54
 Name: RAJAT KUMAR
 Course: EEEE
 Experiment / assignment / tutorial No. IA-I
 Grade: Signature of the Faculty with date

① Sign: Rajatkumar

Q2.

To calculate the current through $4\ \Omega$ resistor using Norton's Theorem.

To calculate:
 I_N , R_N , I_L
 using Norton's Theorem;
 • Norton's Equivalent circuit
 • Norton's Identity:

$$\Rightarrow I_L = \frac{I_N R_N}{R_N + R_L}$$

Sol: Step ①: To Calculate Norton's Current (I_N):
 a) Remove R_L (Load resistance)
 b) Short circuit A & B.

Let, I_1 , I_2 , I_3 be currents flowing in the loops as shown below: (and replacing load resistor R_L ($4\ \Omega$) with short circuit branch)

$I_N = I_1$

②

Sign:
Rajat Kumar

16014224054

RAJAT KUMAR
CE-3 54
EEEE IA-I

Applying KVL at loop ①-

$$\Rightarrow 24 - 4I_1 + I_2 + 3I_3 = 0$$

$$\Rightarrow -4I_1 + I_2 + 3I_3 = -24 \dots \text{①}$$

Applying KVL at loop ②-

$$\Rightarrow 12 + I_1 - 57I_2 + 54I_3 = 0$$

$$\Rightarrow I_1 - 57I_2 + 54I_3 = -12 \dots \text{②}$$

Applying KVL at loop ③-

$$\Rightarrow -10 + 3I_1 + 54I_2 - 59I_3 = 0$$

$$\Rightarrow 3I_1 + 54I_2 - 59I_3 = 10 \dots \text{③}$$

\therefore Solving Equations ①, ②, ③ using calculator:

$$\begin{bmatrix} -4 & 1 & 3 \\ 1 & -57 & 54 \\ 3 & 54 & -59 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -24 \\ -12 \\ 10 \end{bmatrix}$$

$$I_1 = 12.4776 \text{ A}$$

$$I_2 = 6.5448 \text{ A}$$

$$I_3 = 6.4551 \text{ A}$$

$$\therefore I_N = I_1 = 12.4776 \text{ A}$$

$$\boxed{I_N = 12.4776 \text{ A}}$$

③

Sign:
Rajatkumar




SOMAIYA
VIDYAVIHAR UNIVERSITY

16014224054

Batch: C5-3	Roll No.: 54
Name: RAJAT KUMAR	
Course: EEEE	
Experiment / assignment / tutorial No. IA-I	
Grade: <input type="text"/>	Signature of the Faculty with date

Step ② : To Calculate Norton's Resistance (R_N):

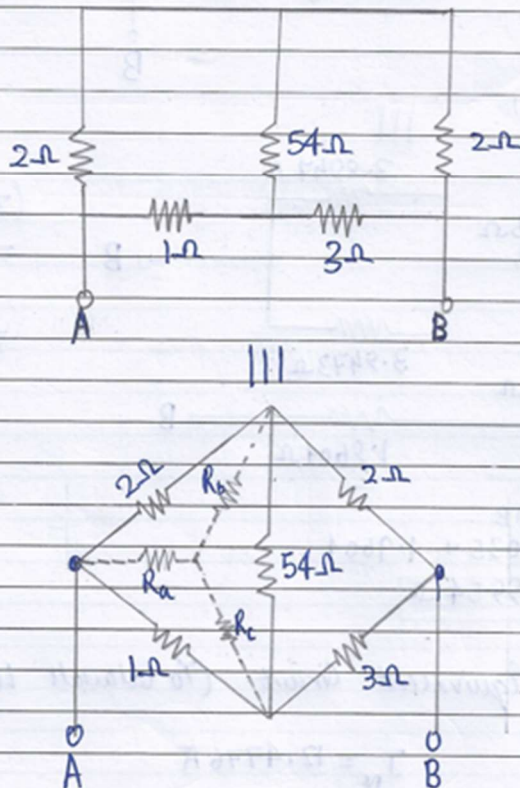- Remove R_L
- Replacing all active sources (here Voltages) with their internal resistances. (i.e. Short ckt)



Using Δ (Delta) \rightarrow λ (Star) Conversion:

$$\therefore R_a = \frac{2 \times 1}{2 + 1 + 54} = \frac{2}{57} = 0.035 \Omega$$

$$\therefore R_b = \frac{2 \times 54}{2 + 1 + 54} = \frac{108}{57} = 1.8947 \Omega$$

$$\therefore R_c = \frac{54 \times 1}{2 + 1 + 54} = \frac{54}{57} = 0.9473 \Omega$$

④



Sign:
Rajatkumar

16014224054

RAJAT KUMAR

C5-3 54
EEEE IA-I

Thus, we get this equivalent circuit-

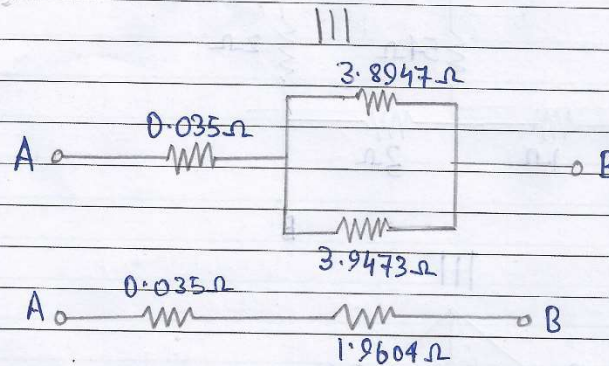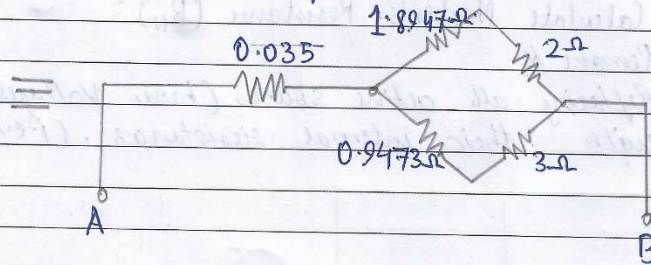


Simplifying-

$$\begin{aligned} & (3.8947 \parallel 3.9473) \\ &= \frac{3.8947 \times 3.9473}{3.8947 + 3.9473} \\ &= 1.9604 \end{aligned}$$

$$\begin{aligned} \therefore R_N &= R_{AB} \\ \therefore R_N &= 0.035 + 1.9604 \\ \therefore R_N &= 1.9954 \Omega \end{aligned}$$

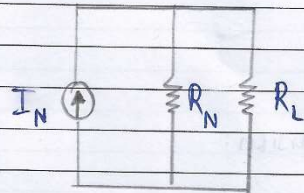Step ③ : Norton's Equivalent Circuit: (To calculate Load Current I_L)



$$\begin{aligned} I_N &= 12.4776 \text{ A} \\ R_N &= 1.9954 \Omega \\ R_L &= 4 \Omega \text{ (Given)} \end{aligned}$$

Using, Norton's Identity -

$$\begin{aligned} \Rightarrow I_L &= \frac{I_N \times R_N}{R_N + R_L} = \frac{12.4776 \times 1.9954}{1.9954 + 4} = \frac{24.8978}{5.9954} \\ \therefore I_L &= 4.1528 \text{ A} \end{aligned}$$

Tabulate the results as shown in the table below.

Parameter	Theoretical value	Simulated value
Norton's Current (I_N)	12.4776 A	12.4776 A
Norton's Resistance (R_N)	1.9954 Ω	1.9955 Ω
Load Current (I_L)	4.1528 A	4.1528 A

Q5. Explain the principle & working of Megger with a neat labelled diagram.
 If last two digits of roll no are from 41 to 60, attempt Q5

16014224054

Batch: C5-3 Roll No.: 54
 Name: RAJAT KUMAR
 Course: EEEE
 Experiment / assignment / tutorial No. IA-I
 Grade: Signature of the Faculty with date

⑤ Sign: Rajat Kumar

Q5. Explain the principle and working principle of Megger with a neat labelled diagram.

Sol: The megger is an instrument used for measuring the insulation resistance of electrical equipment such as cables, transformers, and motor windings. The test is crucial for ensuring safety and efficient operation by identifying potential faults in insulation. If resistance of insulation is high, pointer coil deflects towards infinity, if low, pointer indicates zero resistance. Accuracy of megger is high as compared to other instruments. Combination of both generator & ohmmeter is basically a megger.

Principle:
 The principle of a megger is based on Ohm's Law and principle of electromagnetic induction. When a voltage is applied across an electrical circuit, a current flows through the insulation. By measuring the resulting current, the megger calculates the insulating resistance. A megger typically applies a high DC voltage (500V → 5kV) to the insulation, and the resistance is calculated based on current generated.

Circuit Diagram-

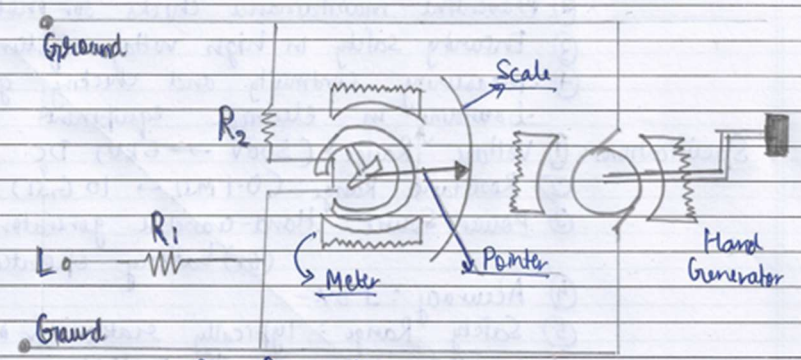


Fig. Basic Megger Circuit

<p>⑥</p>	<p>Sign: Rajat Kumar</p>	<p>16014244054 RAJAT KUMAR CE-3 54 EEEE IA-I</p>
<p><u>WORKING:</u></p>		
<p>① Initial Setup: The test terminals are connected to the device which is have insulation to be tested. The terminals marked "Line" and "Earth" are connected to the ends of the insulation being measured, while "Guard" may be used to remove leakage effects from the measurement.</p> <p>② Voltage Generation: When the handle is cranked, the generator in the megger produces a high DC voltage. For modern meggers, batteries may replace the mechanical generator.</p> <p>③ Resistance Measurement: The generated voltage is applied across the insulation under test. The insulation typically allows a small amount of current to pass. The current measured is by the PMMC meter inside megger.</p> <p>④ Meter Deflection: The current passing through the circuit causes deflection in the scale of the meter, indicating the insulation resistance. A higher deflection means lower resistance, indicating poor insulation, while little or no deflection indicates high insulation resistance which is desired.</p>		
<p><u>Applications:</u></p> <ul style="list-style-type: none"> ① Testing insulation resistance in electrical cables. ② Preventive maintenance checks for motors. ③ Ensuring safety in high voltage systems. ④ Measuring continuity and checking ground bonding in electrical equipment. 		
<p><u>Specifications:</u></p> <ul style="list-style-type: none"> ① Voltage Range: (500V → 5kV) DC ② Resistance Range: (0.1 MΩ → 10 GΩ) ③ Power Source: Hand-cranked generator (or) battery operated. ④ Accuracy: ± 5%. ⑤ Safety Range: Typically rated for individual or field use with IP protection. 		